

# Digital Logic


## Day 6

[uarch.space](https://uarch.space)

[uarch.space/slides/day6.pdf](https://uarch.space/slides/day6.pdf)
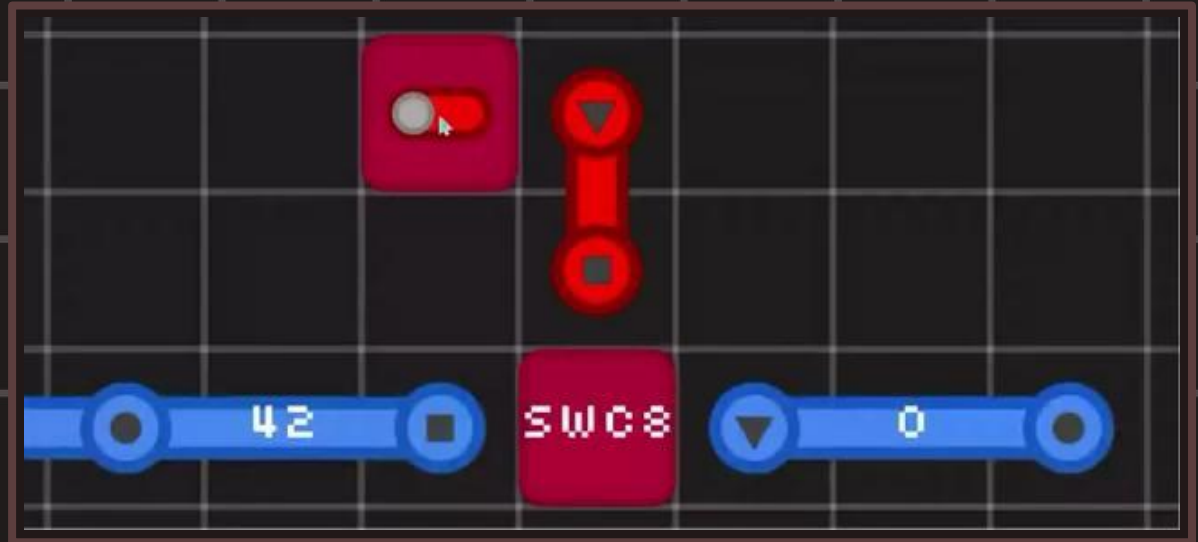
# Switch component

The Switch component allows enables or disables an 8-bit wire.




# ALU (Arithmetic Logic Unit)

The ALU is like a calculator.

Like on a calculator, you can select what operation to perform and what your operands are.

All inputs are 8 bit.

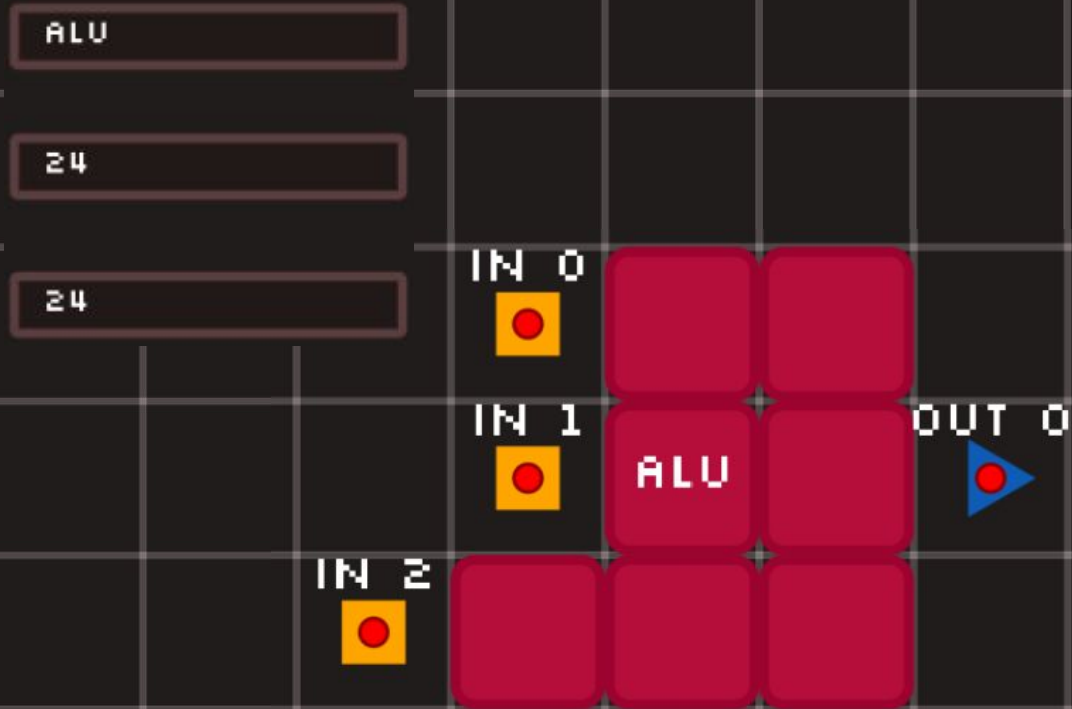

# Bitwise Operators

Bitwise operations are like the existing logic gates you know, except they operate on 8 bits at a same time.

Only columns where:  
(1 AND 1) outputs 1

|   |   |   |   |   |   |   |   |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |
|---|---|---|---|---|---|---|---|

AND (&)

|   |   |   |   |   |   |   |   |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
|---|---|---|---|---|---|---|---|

Bitwise AND

# Bitwise Operators

|   |   |   |   |   |   |   |   |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |
|---|---|---|---|---|---|---|---|

Bitmasked Right Shift (>>)

|   |   |   |   |   |   |   |   |
|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 |
|---|---|---|---|---|---|---|---|

Bitmasked Left Shift (<<)

|   |   |   |   |   |   |   |   |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
|---|---|---|---|---|---|---|---|

NOT (~)

(<<) is equivalent to multiplying by two.

(>>) is equivalent to dividing by two.

# ALU (Arithmetic Logic Unit)

These are the operations that we will use.

IDENTITY just outputs the first operand without any calculation.

Some operations ignore the second operand entirely.

|     |          |                                 |
|-----|----------|---------------------------------|
| 000 | ADD      | Adds the two operands           |
| 001 | AND      | Bitwise ANDs the two operands   |
| 010 | OR       | Bitwise ORs the two operands    |
| 011 | XOR      | Bitwise XORs the two operands   |
| 100 | NOT      | Inverts the first operand       |
| 101 | SHR      | Bit Shift operand 1 right 1 bit |
| 110 | SHL      | Bit Shift operand 1 left 1 bit  |
| 111 | IDENTITY | Output operand 1                |

# Solutions:

[uarch.space/solutions/day6.pdf](https://uarch.space/solutions/day6.pdf)