

Digital Logic

Day 2

uarch.space

now you try

XOR GATE

A XOR gate has two inputs  and one output . It only on if the inputs are different.

Click the  icon to place components down.

Click the play  button to run the tests. If your circuit is correct, it should pass 4/4 tests.

A	B	Y
		
		
		
		

now you try

XNOR GATE

A XNOR gate has two inputs and one output . It is the inversion of the XOR gate, just like how NAND inverts AND and NOR inverts OR.



A	B	Y
		
		
		
		

Challenge

- In the final level, you have 8 inputs. You should only output **ON** if an **ODD** number of inputs are on.
- For example, if only 1 input is **ON**, output **ON**, since 1 is odd. If 4 inputs are **ON** output **OFF**. The order of the inputs do not matter.

